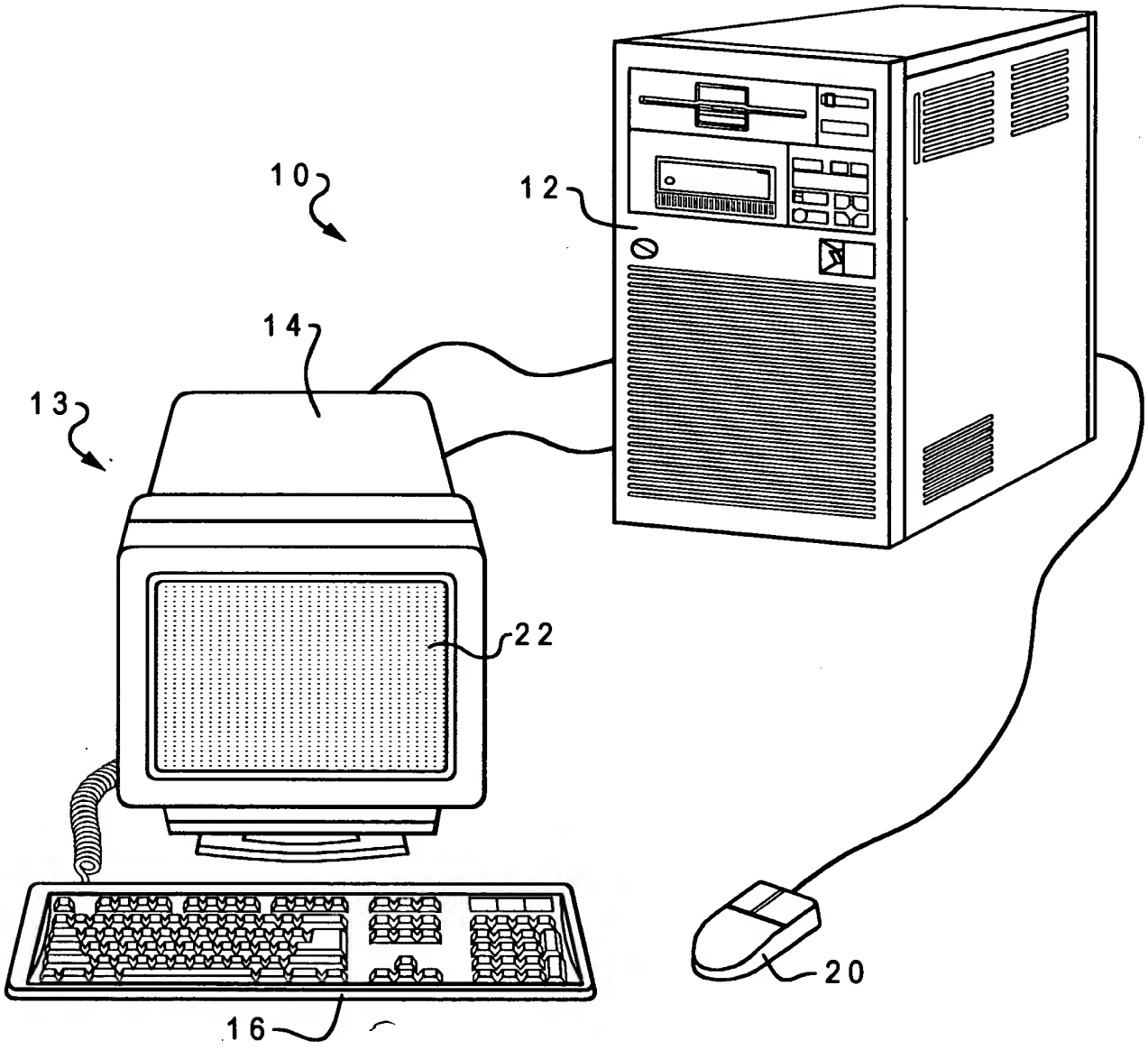

Fig. 1

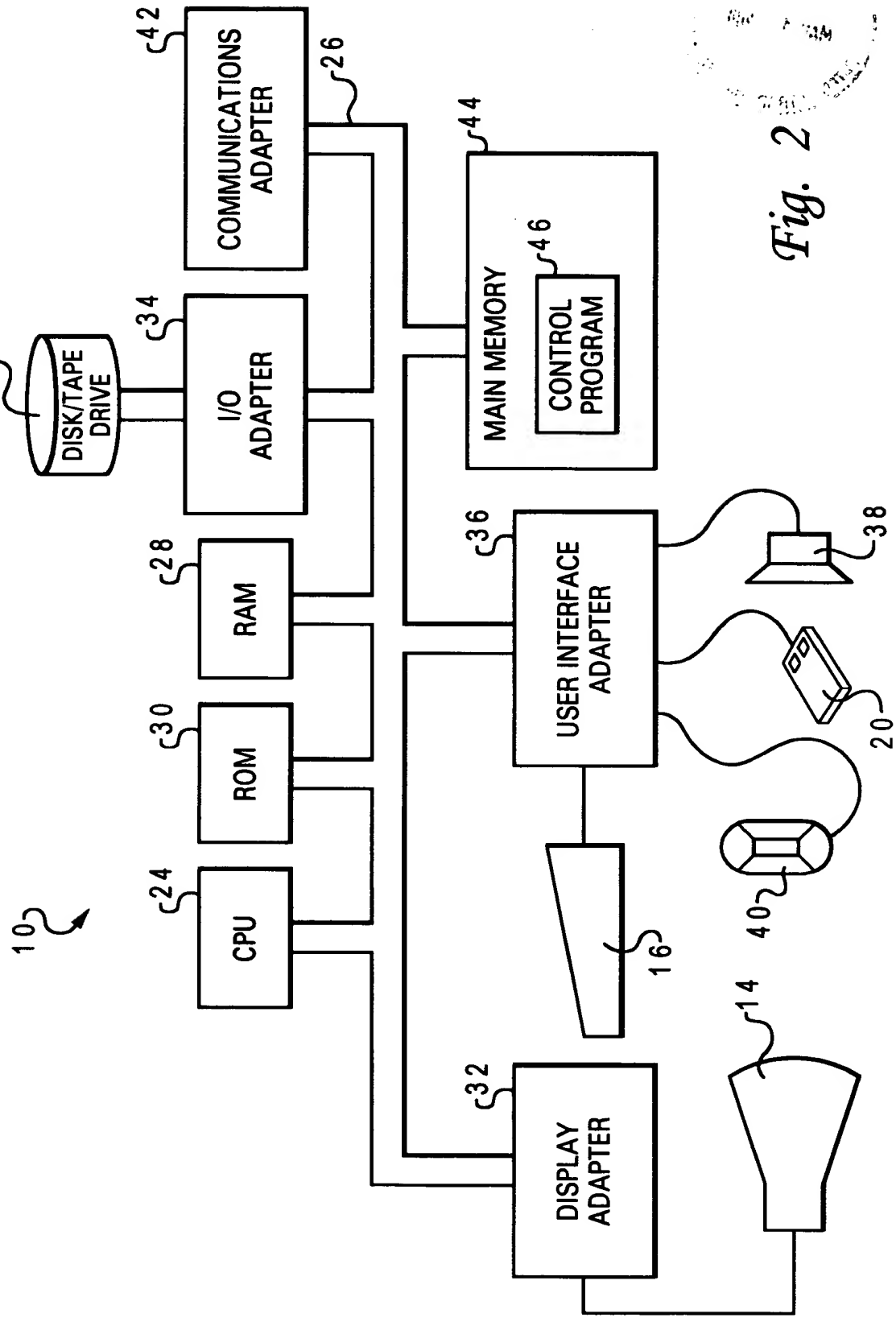
10
CPU
24
ROM
30
RAM
28
I/O ADAPTER
34
DISK/TAPE DRIVE
33
COMMUNICATIONS ADAPTER
42
26
MAIN MEMORY
44
CONTROL PROGRAM
46
USER INTERFACE ADAPTER
36
DISPLAY ADAPTER
32
16
14
40
20
38

Fig. 2

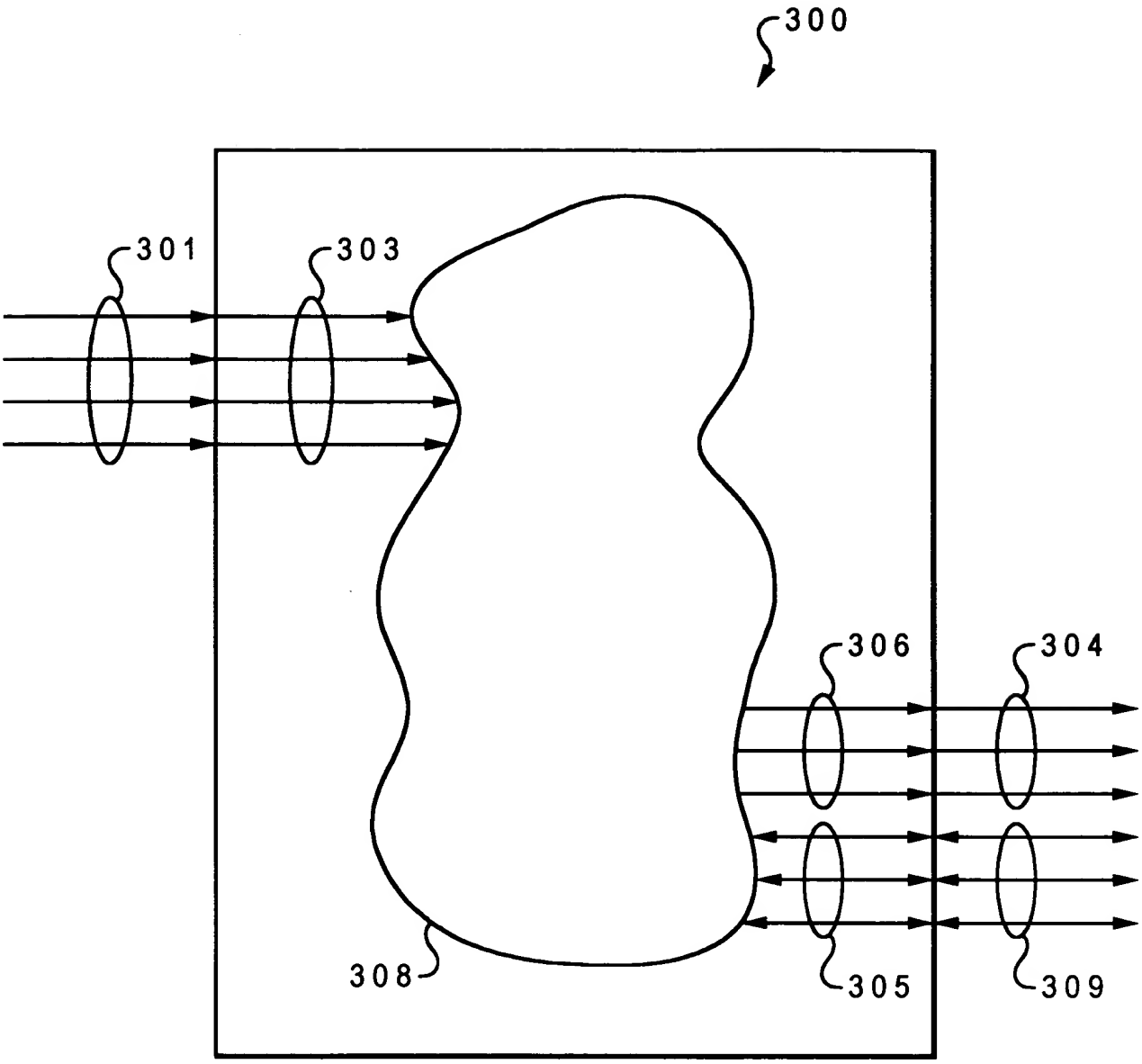

Fig. 3A

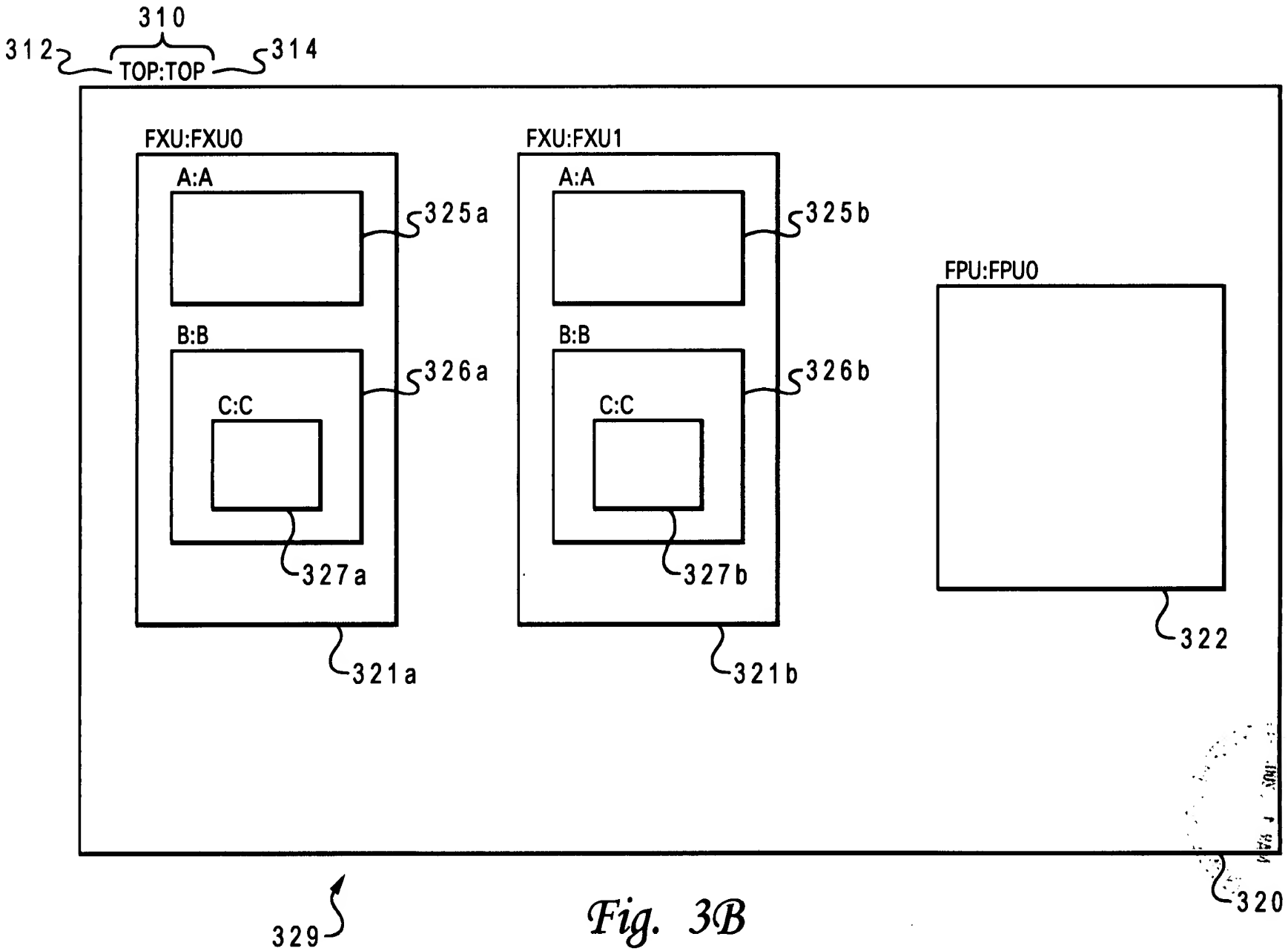
310
312
TOP:TOP
314
FXU:FXU0
A:A
325a
B:B
326a
C:C
327a
321a
FXU:FXU1
A:A
325b
B:B
326b
C:C
327b
321b
FPU:FPU0
322
320
329

Fig. 3B

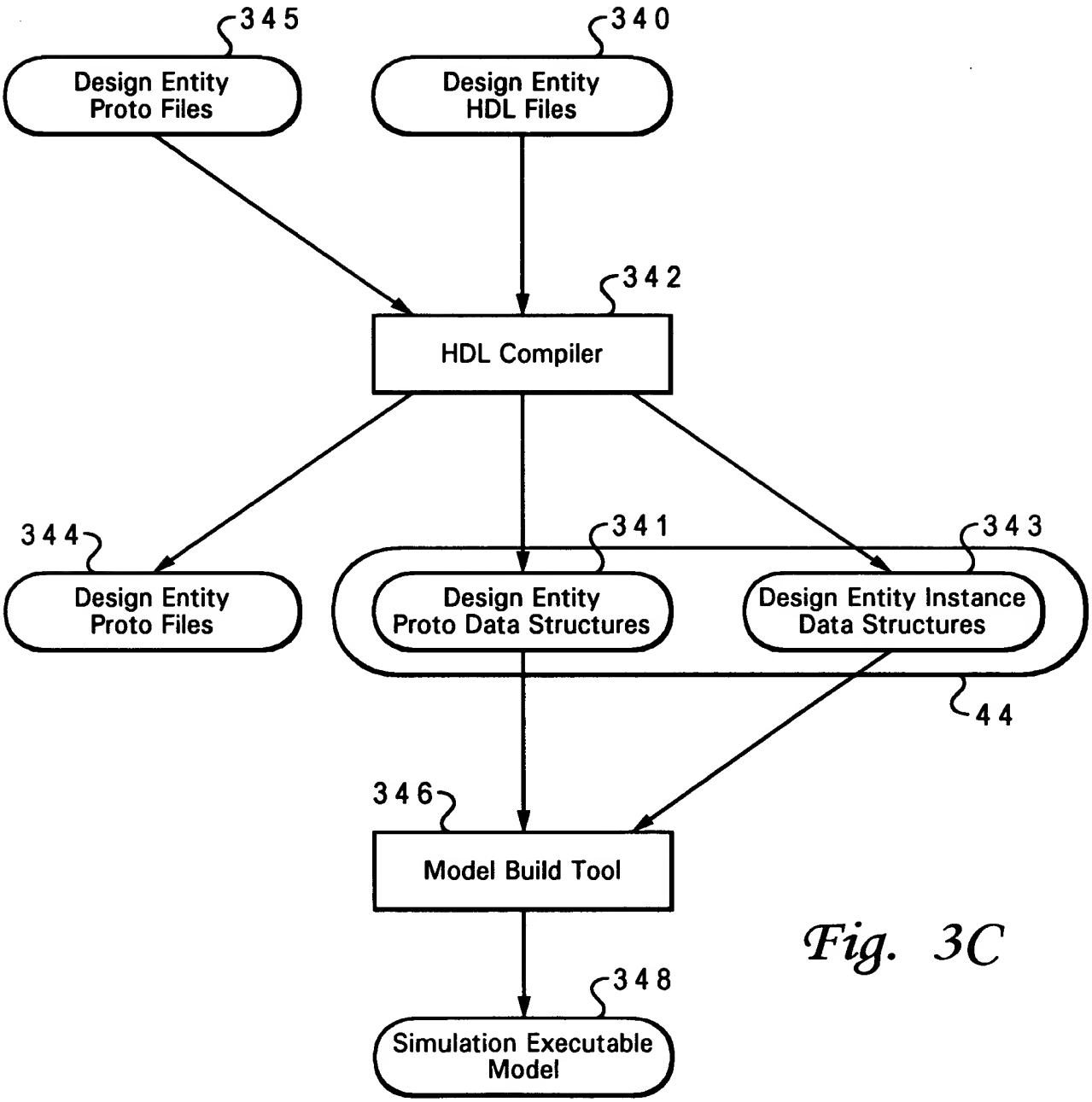
345
Design Entity Proto Files
340
Design Entity HDL Files
342
HDL Compiler
344
Design Entity Proto Files
341
Design Entity Proto Data Structures
343
Design Entity Instance Data Structures
44
346
Model Build Tool
348
Simulation Executable Model

Fig. 3C

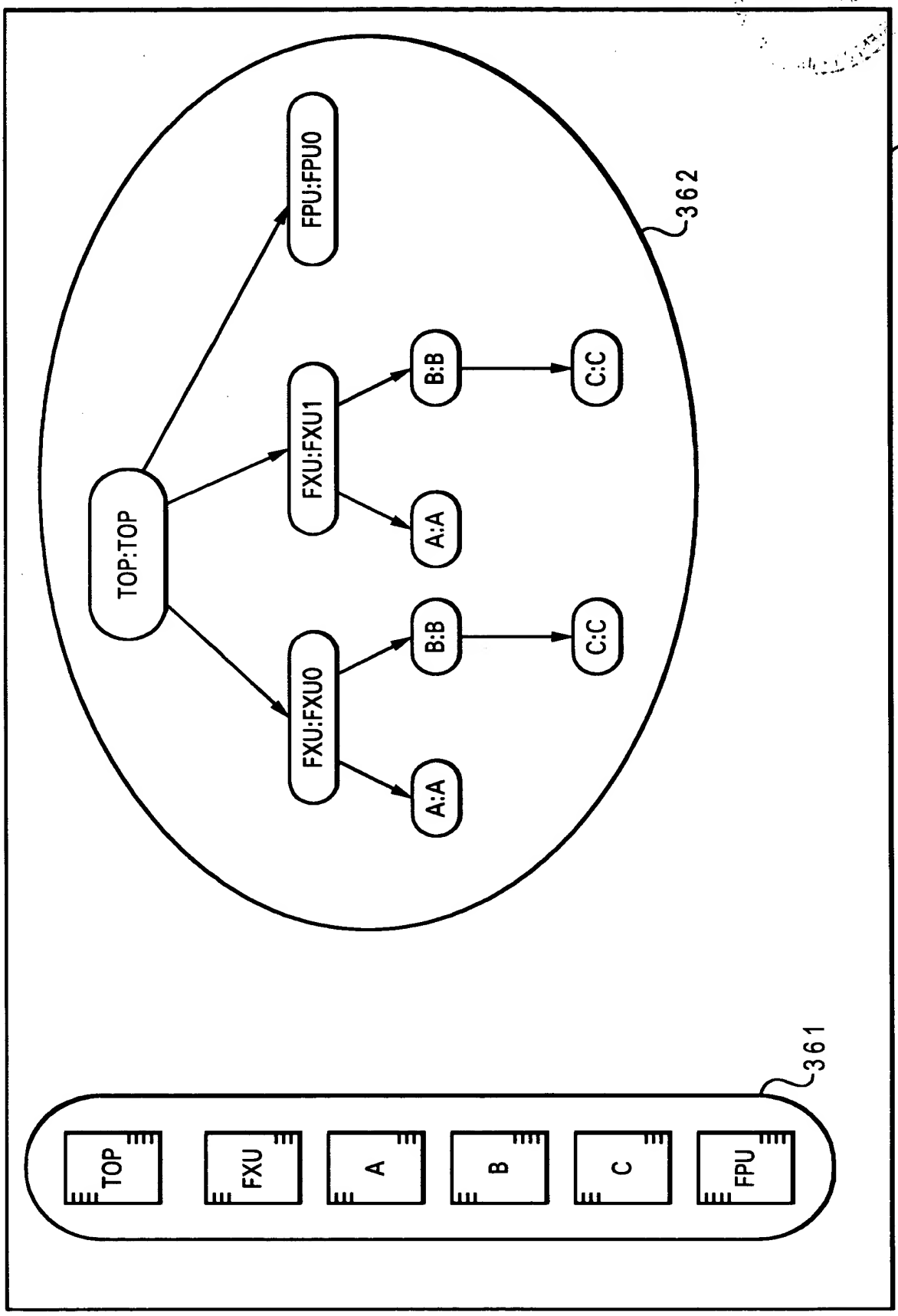
TOP
FXU
A
B
C
FPU
361
TOP:TOP
FXU:FXU0
FXU:FXU1
FPU:FPU0
A:A
B:B
C:C
A:A
B:B
C:C
362
44

Fig. 3D

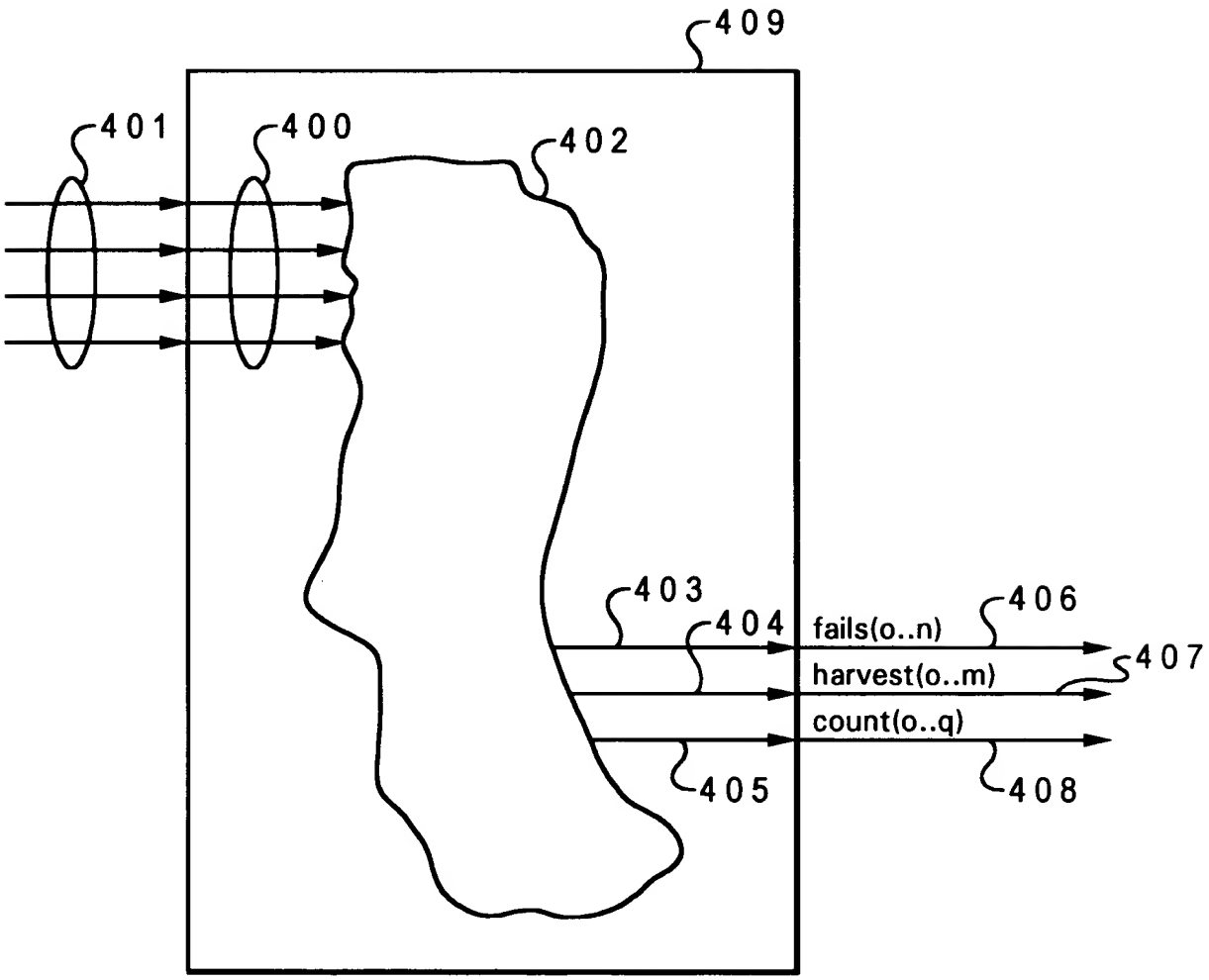
409
401
400
402
403
404
406
fails(o..n)
407
harvest(o..m)
count(o..q)
405
408

Fig. 4A

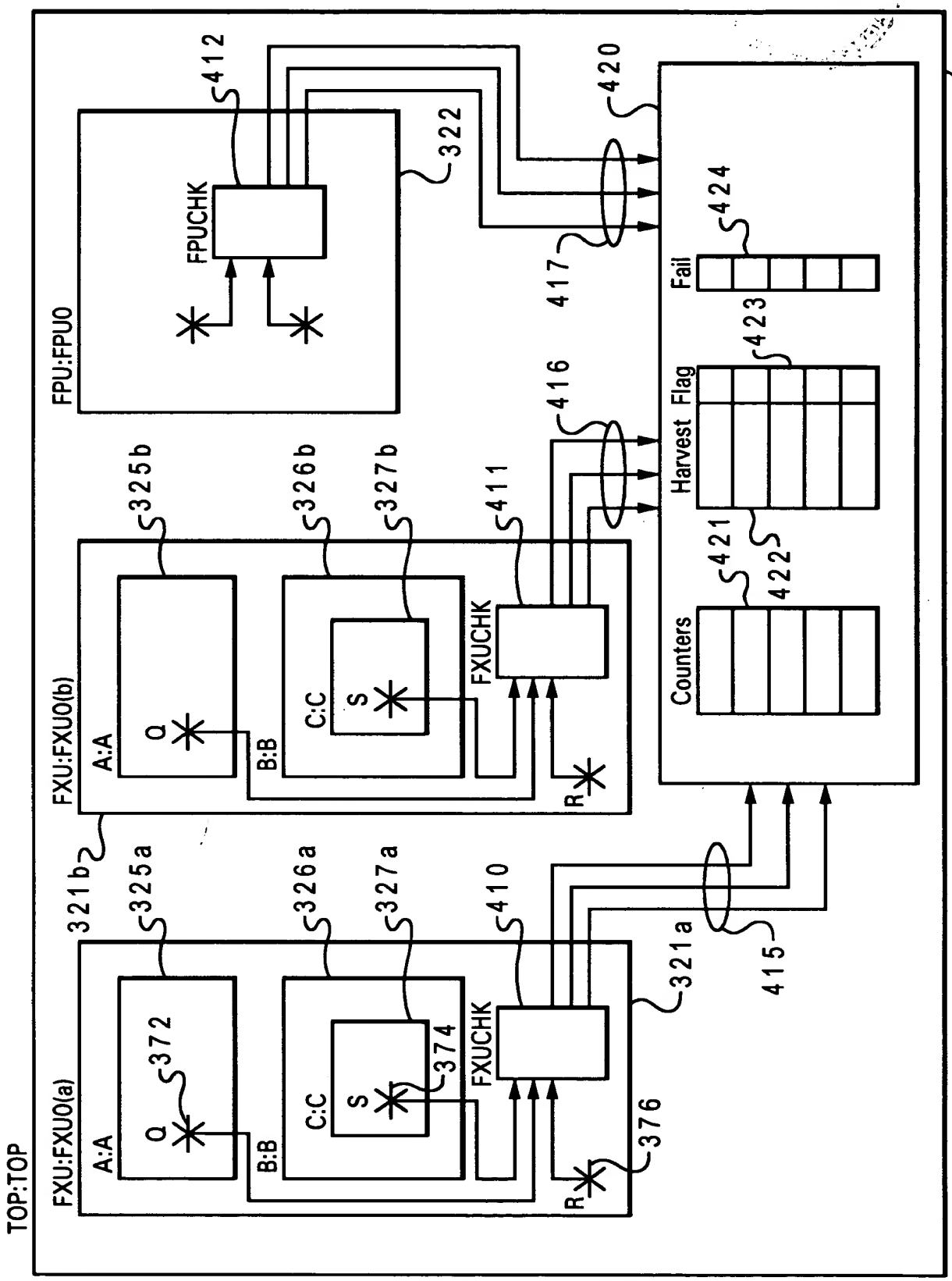
TOP:TOP
FXU:FXU0(a)
A:A
Q
372
B:B
C:C
S
374
FXUCHK
R
376
321b
325a
326a
327a
410
321a
415
FXU:FXU0(b)
325b
326b
327b
411
416
FPU:FPU0
FPUCHK
412
322
417
420
329
Fail
424
Harvest Flag
423
Counters
421
422

Fig. 4B

```
ENTITY FXUCHK IS

    PORT(   S_IN        :     IN std_ulogic;
            Q_IN        :     IN std_ulogic;
            R_IN        :     IN std_ulogic;
            clock       :     IN std_ulogic;
            fails       :     OUT std_ulogic_vector(0 to 1);
            counts      :     OUT std_ulogic_vector(0 to 2);
            harvests    :     OUT std_ulogic_vector(0 to 1);
        );

--!! BEGIN
--!! Design Entity: FXU;

--!! Inputs
--!! S_IN        =>      B.C.S;
--!! Q_IN        =>      A.Q;
--!! R_IN        =>      R;
--!! CLOCK       =>      clock;
--!! End Inputs

--!! Fail Outputs;
--!! 0 : "Fail message for failure event 0";
--!! 1 : "Fail message for failure event 1";
--!! End Fail Outputs;

--!! Count Outputs;
--!! 0 : <event0> clock;
--!! 1 : <event1> clock;
--!! 2 : <event2> clock;
--!! End Count Outputs;

--!! Harvest Outputs;
--!! 0 : "Message for harvest event 0";
--!! 1 : "Message for harvest event 1";
--!! End Harvest Outputs;

--!! End;

ARCHITECTURE example of FXUCHK IS

BEGIN

    ... HDL code for entity body section ...

END;
```

450 452 453 454 455 456 457 451 458 440

Fig. 4C

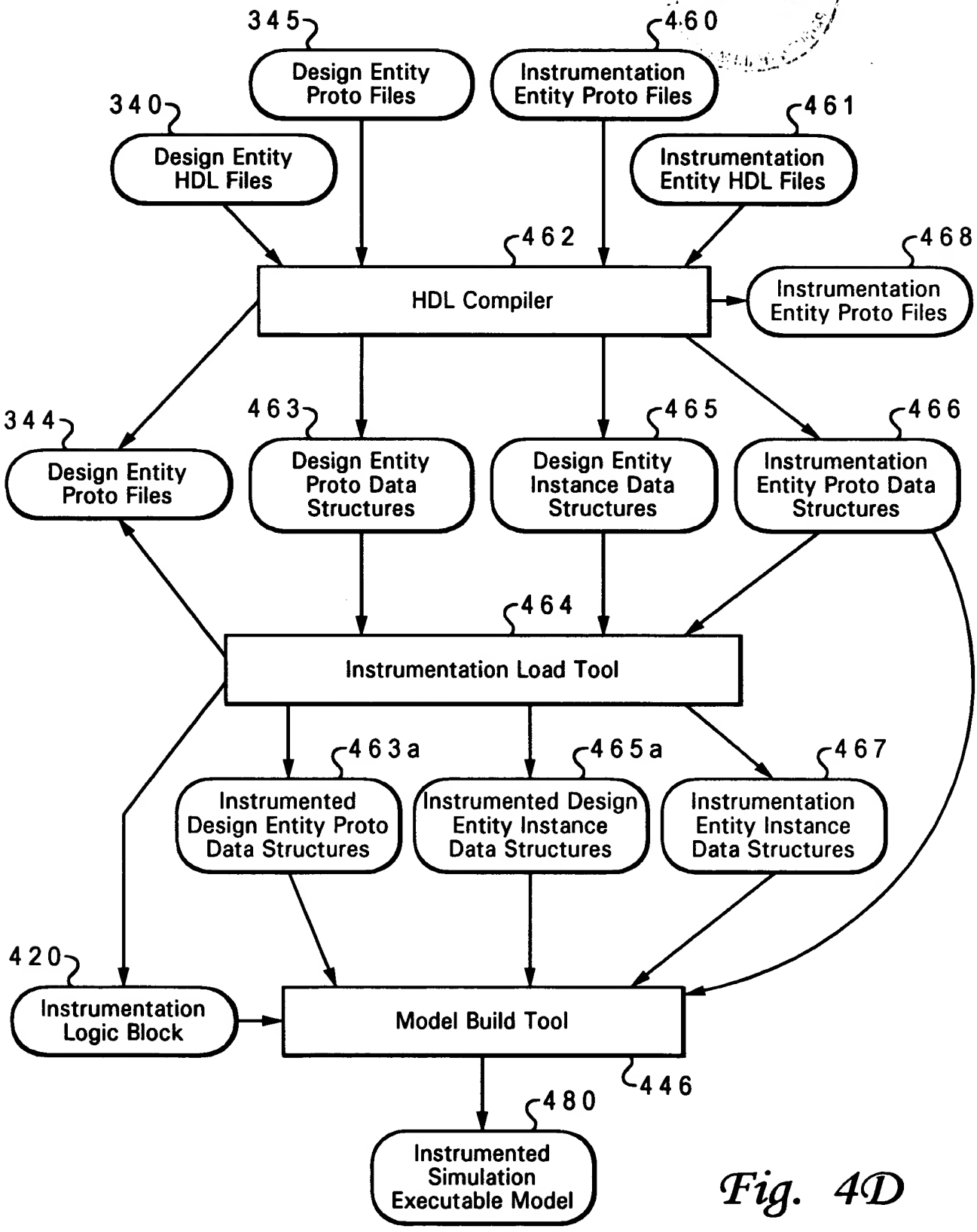
345
Design Entity Proto Files
460
Instrumentation Entity Proto Files
340
Design Entity HDL Files
461
Instrumentation Entity HDL Files
462
HDL Compiler
468
Instrumentation Entity Proto Files
344
Design Entity Proto Files
463
Design Entity Proto Data Structures
465
Design Entity Instance Data Structures
466
Instrumentation Entity Proto Data Structures
464
Instrumentation Load Tool
463a
Instrumented Design Entity Proto Data Structures
465a
Instrumented Design Entity Instance Data Structures
467
Instrumentation Entity Instance Data Structures
420
Instrumentation Logic Block
Model Build Tool
446
480
Instrumented Simulation Executable Model

Fig. 4D

44
482
481
TOP:TOP
FXU:FXU0
FXU:FXU1
FPU:FPU0
A:A
FXUCHK
B:B
C:C
FPUCHK
TOP
FXU
A
B
C
FPU
FXUCHK
FPUCHK

Fig. 4E

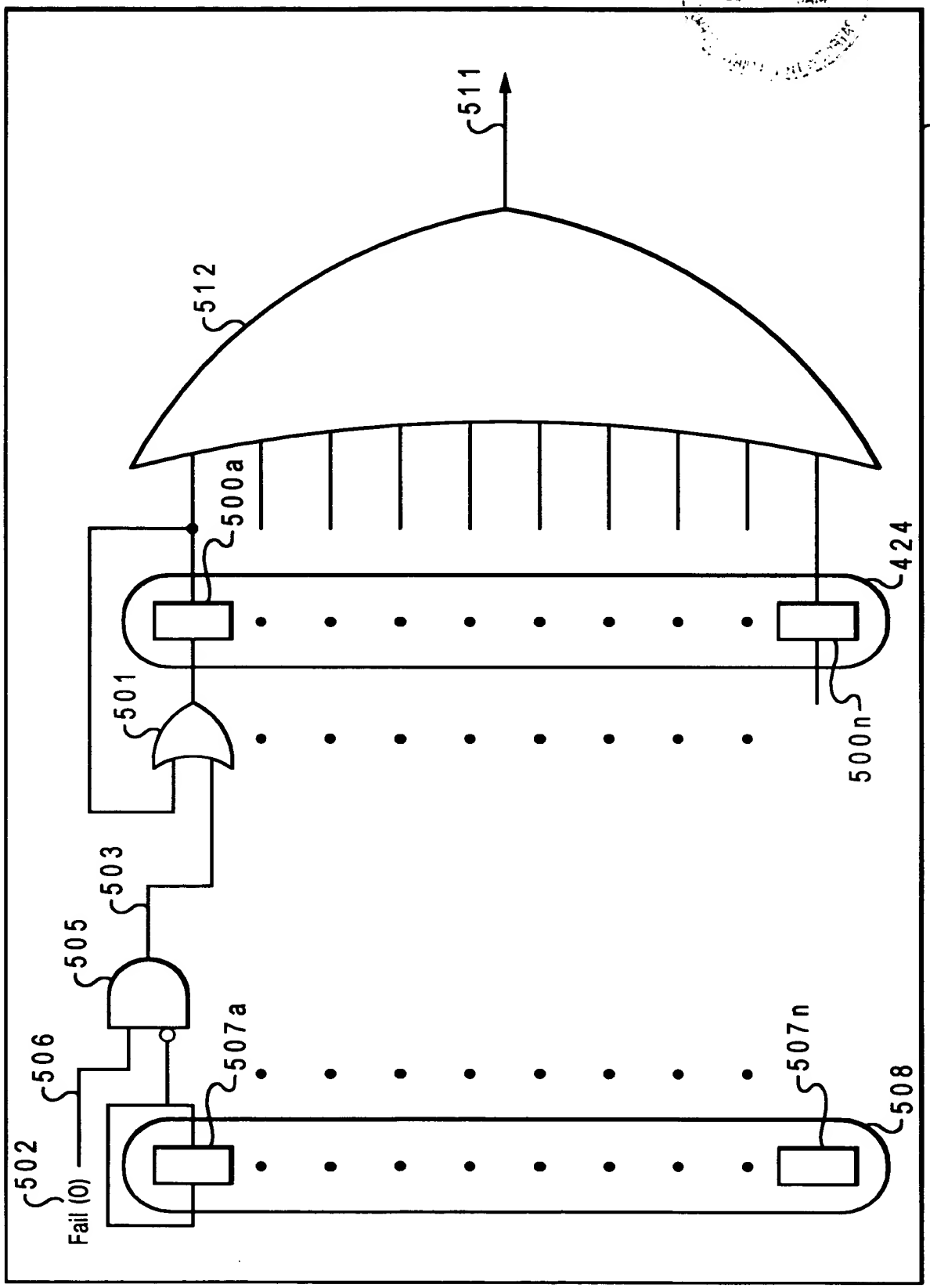
511
420
512
500a
424
501
500n
503
505
506
507a
507n
508
502
Fail (0)

Fig. 5A

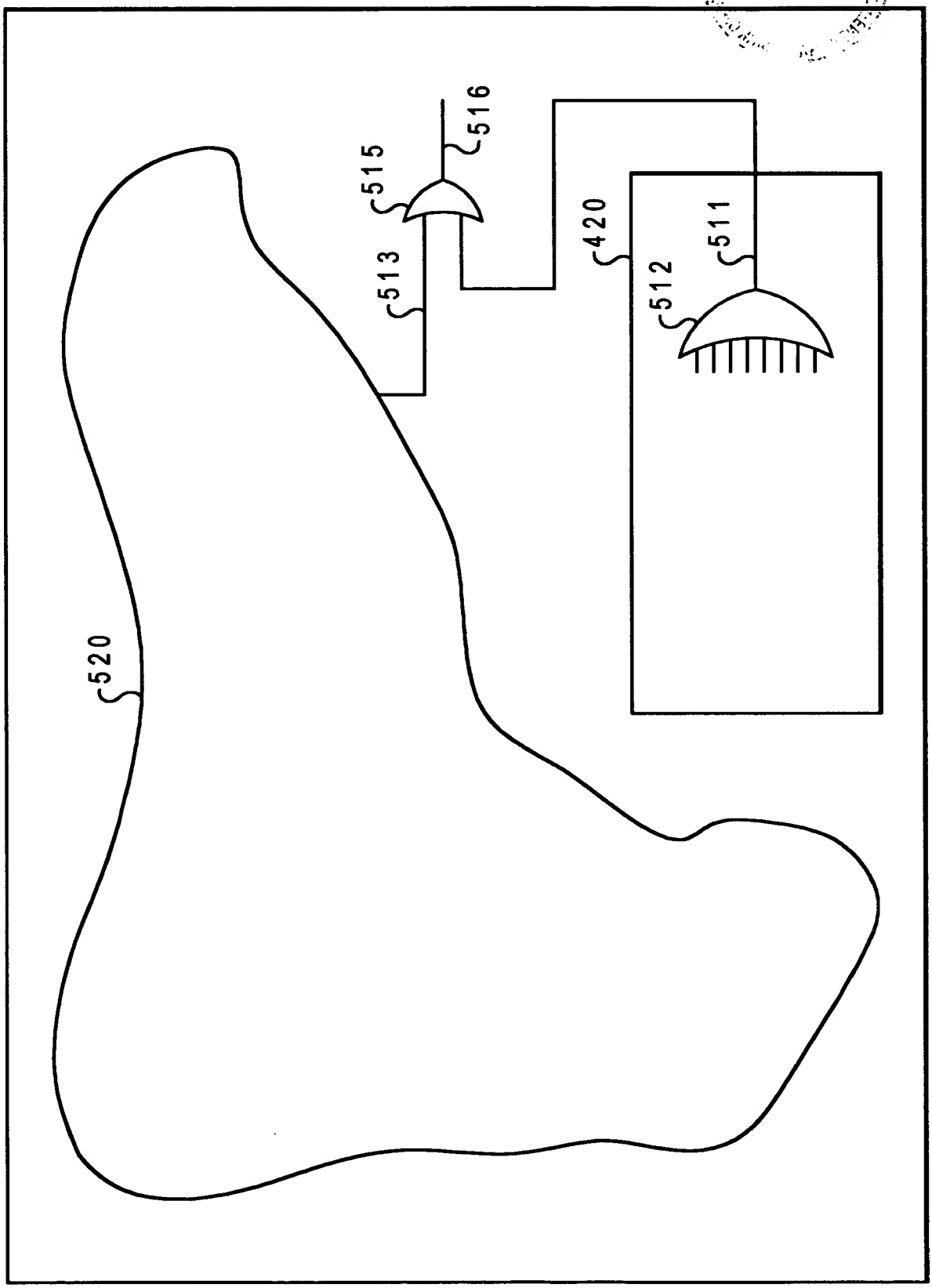

Fig. 5B

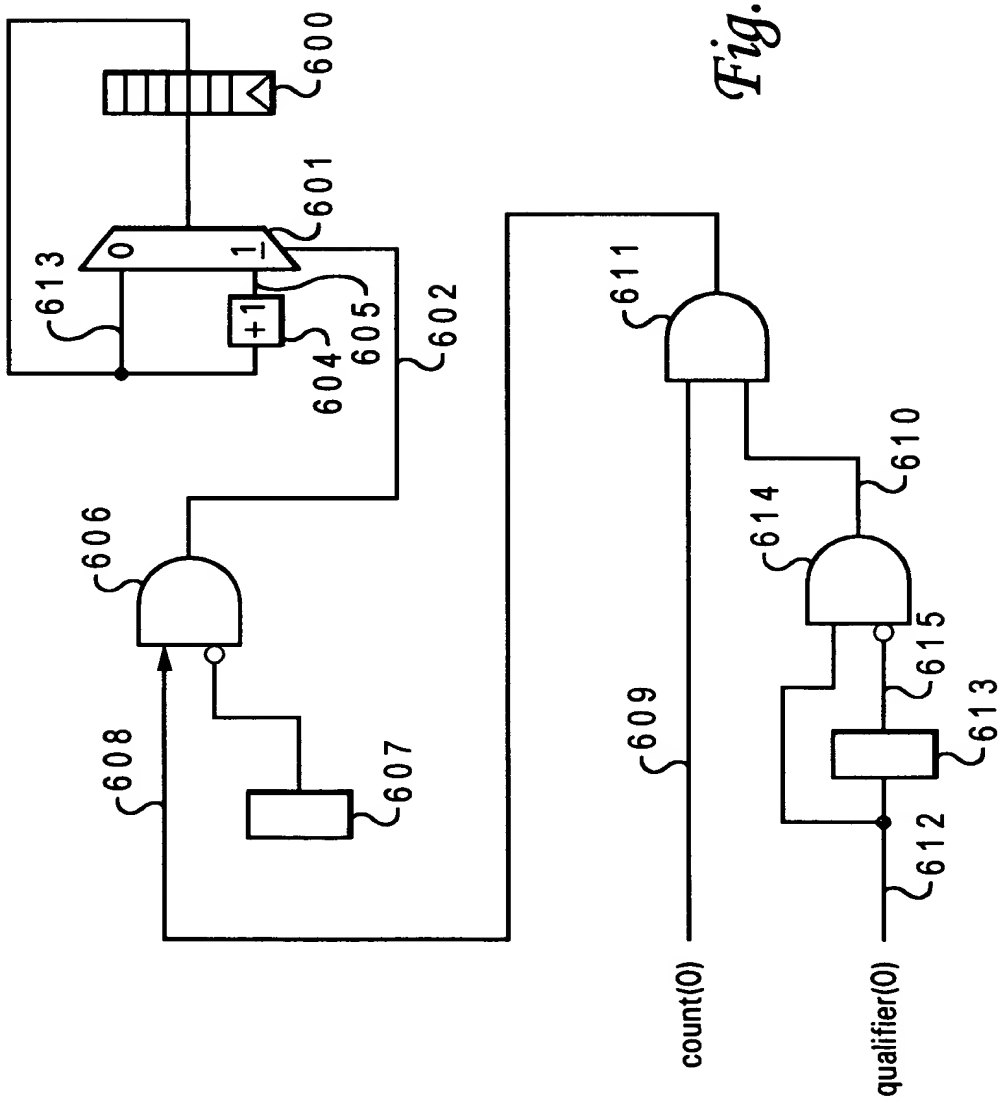
600
601
0
1
613
+1
604
605
602
606
608
607
611
609
610
614
615
613
612
count(0)
qualifier(0)

Fig. 6A

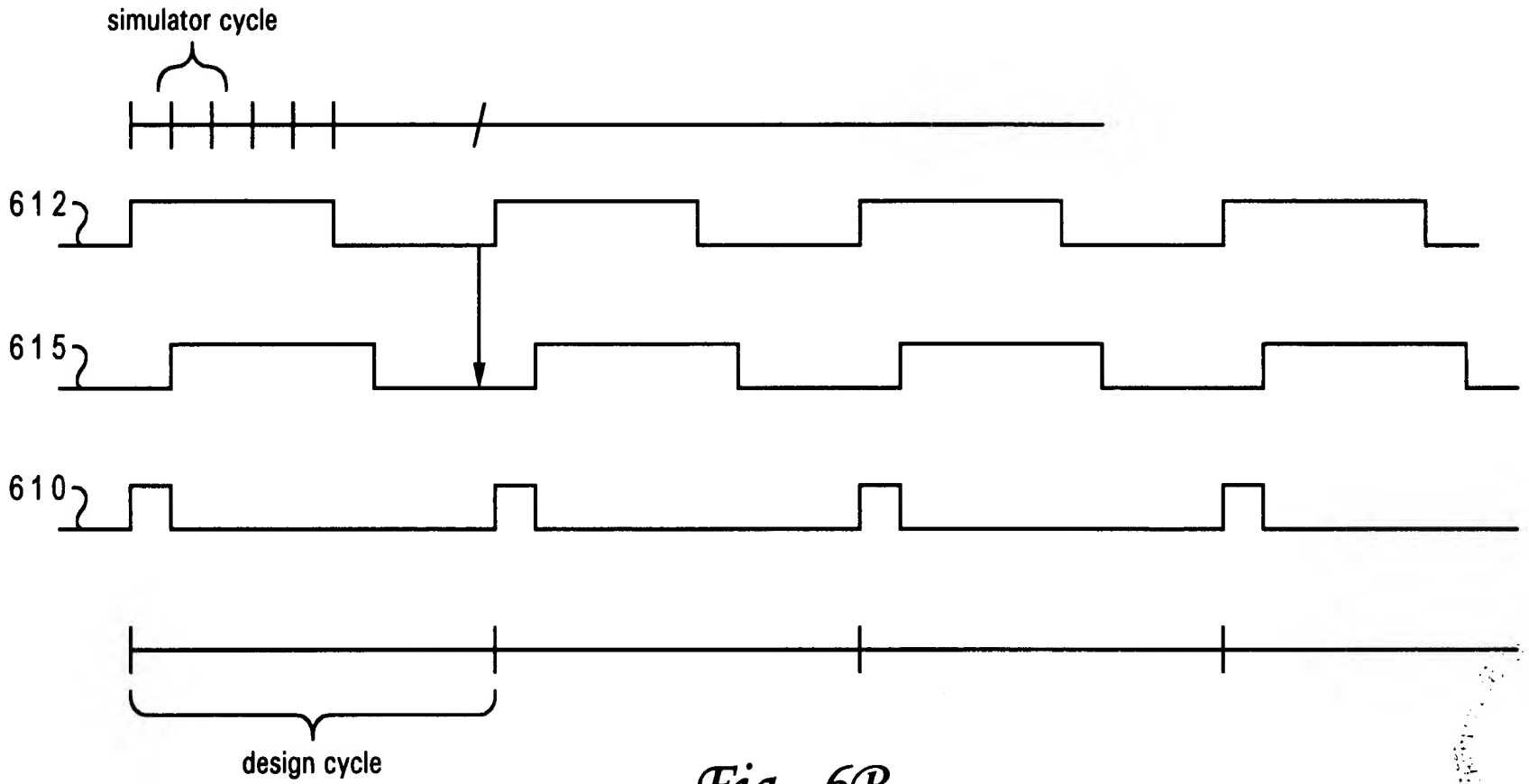

Fig. 6B

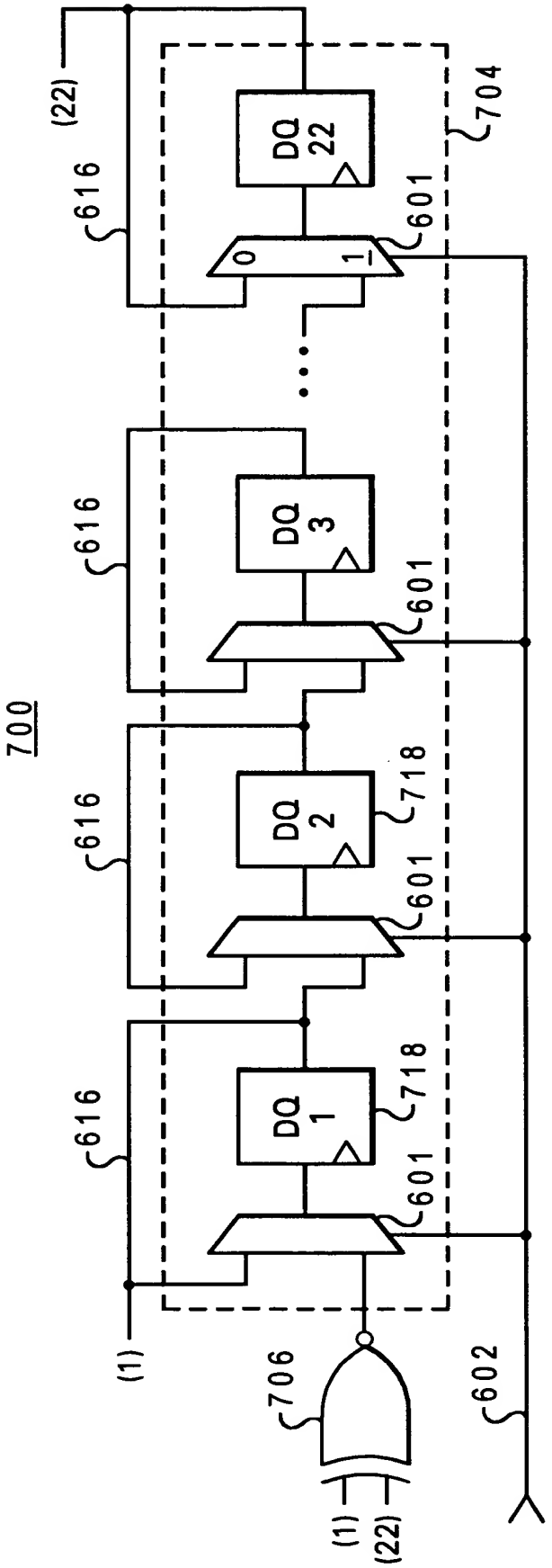

Fig. 7

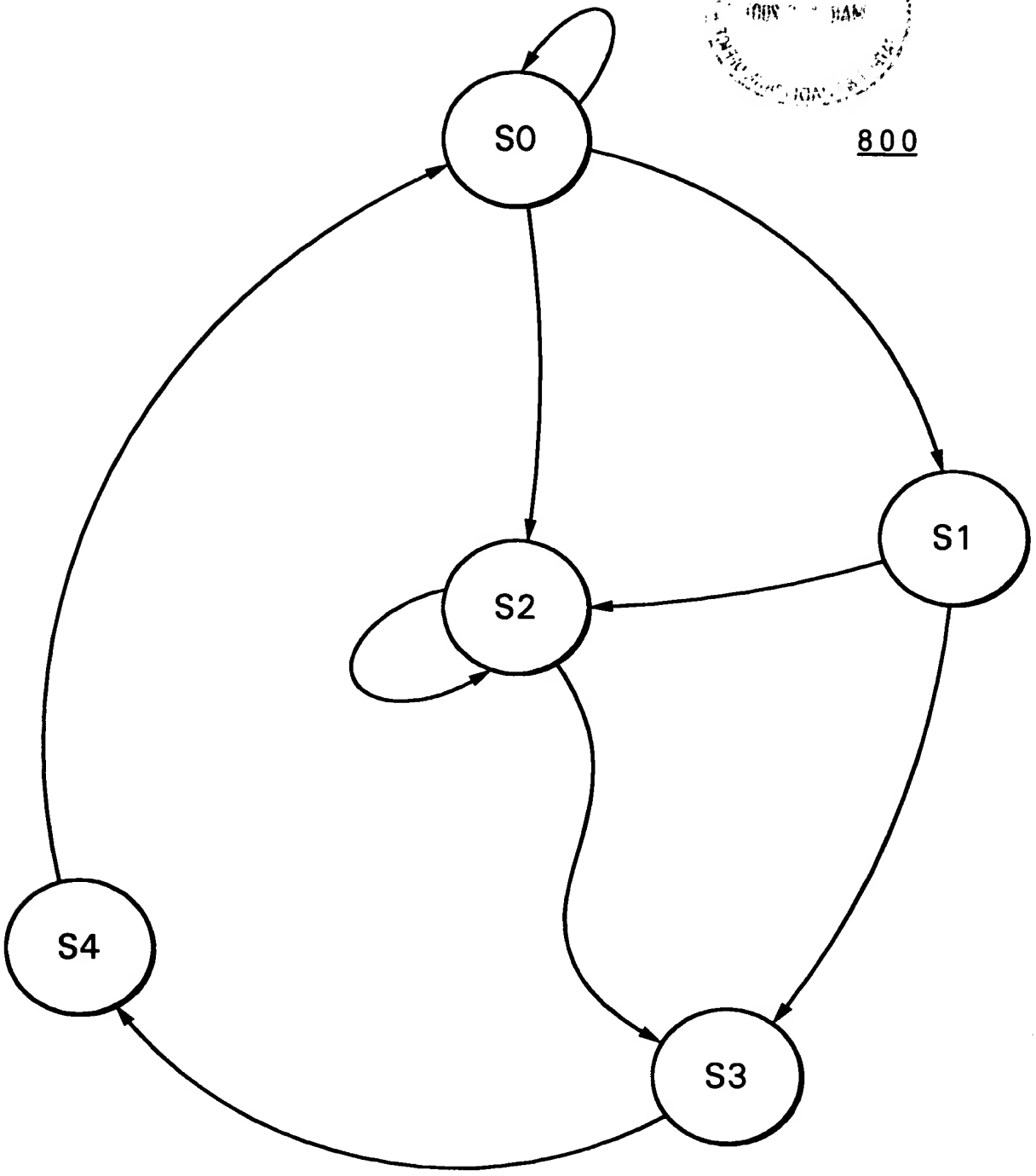

Fig. 8A
Prior Art

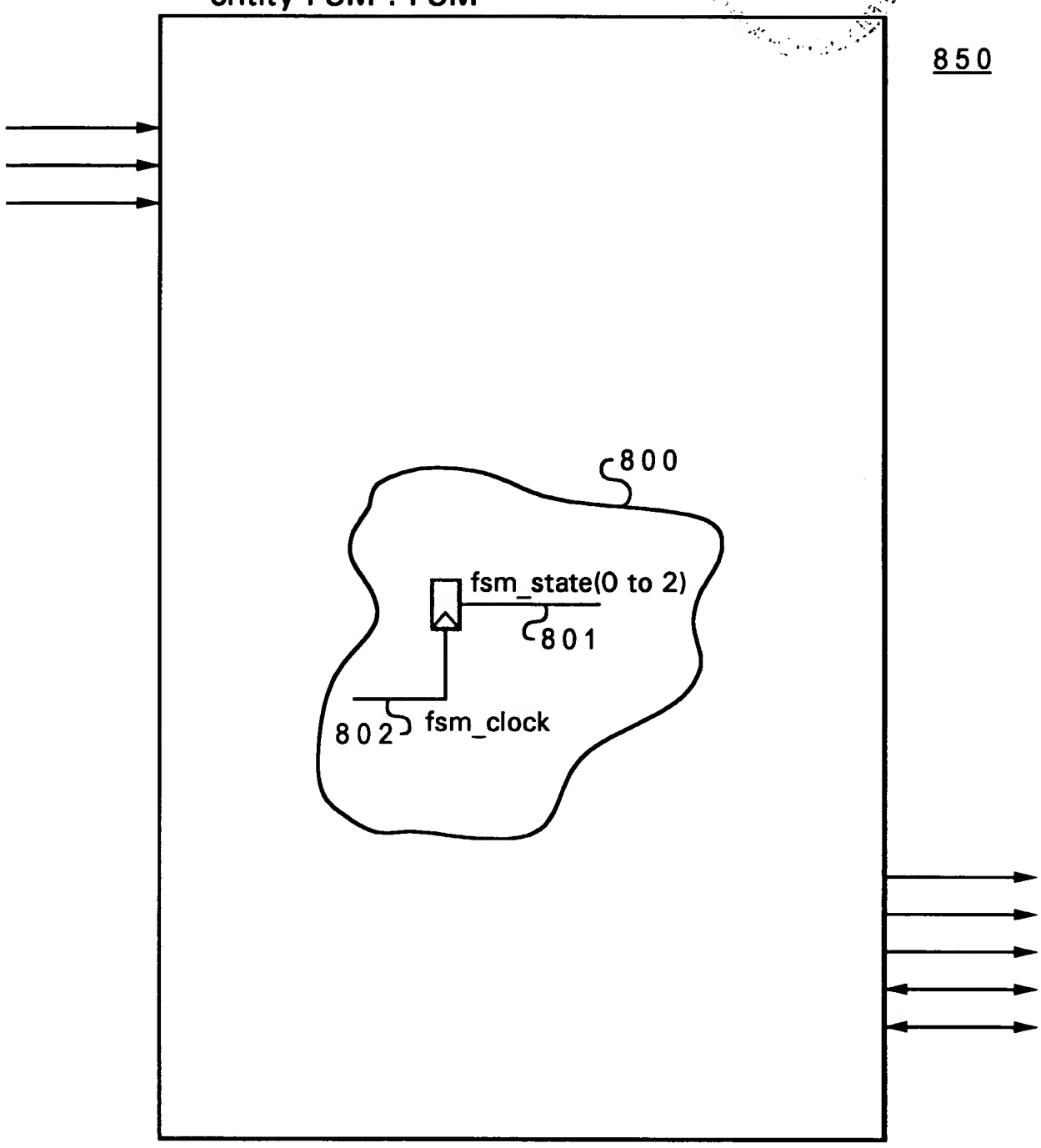

Fig. 8B
Prior Art

```
ENTITY FSM IS

    PORT(
            ....ports for entity fsm....
        );

    ARCHITECTURE FSM OF FSM IS

    BEGIN

            ... HDL code for FSM and rest of the entity ...

            fsm_state(0 to 2) <= ... Signal 801 ...

853 --!! Embedded FSM : examplefsm;
859 --!! clock        : (fsm_clock);
854 --!! state_vector : (fsm_state(0 to 2));
855 --!! states       : (S0, S1, S2, S3, S4);
856 --!! state_encoding : ('000', '001', '010', '011', '100');
    --!! arcs         : (S0 => S0, S0 => S1, S0 => S2,
857 --!!                 (S1 => S2, S1 => S3, S2 => S2,
    --!!                 (S2 => S3, S3 => S4, S4 => S0);
858 --!! End FSM;

                ,
                ,
                ,
                ,
                ,
                ,
                ,

    END;
```

852 860

Fig. 8C

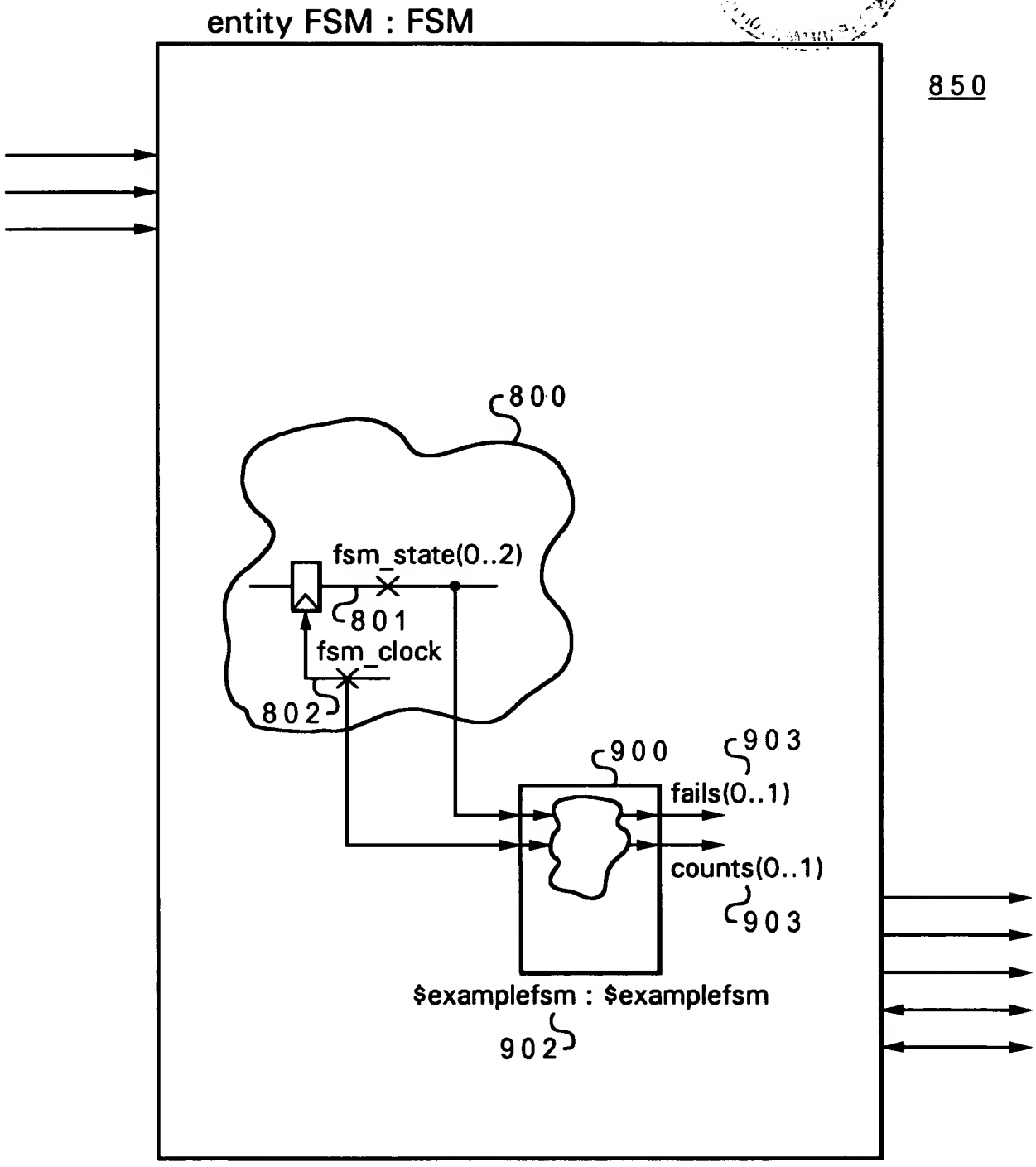
entity FSM : FSM
850
800
fsm_state(0..2)
801
fsm_clock
802
900
903
fails(0..1)
counts(0..1)
903
$examplefsm : $examplefsm
902

Fig. 9

Fig. 10A

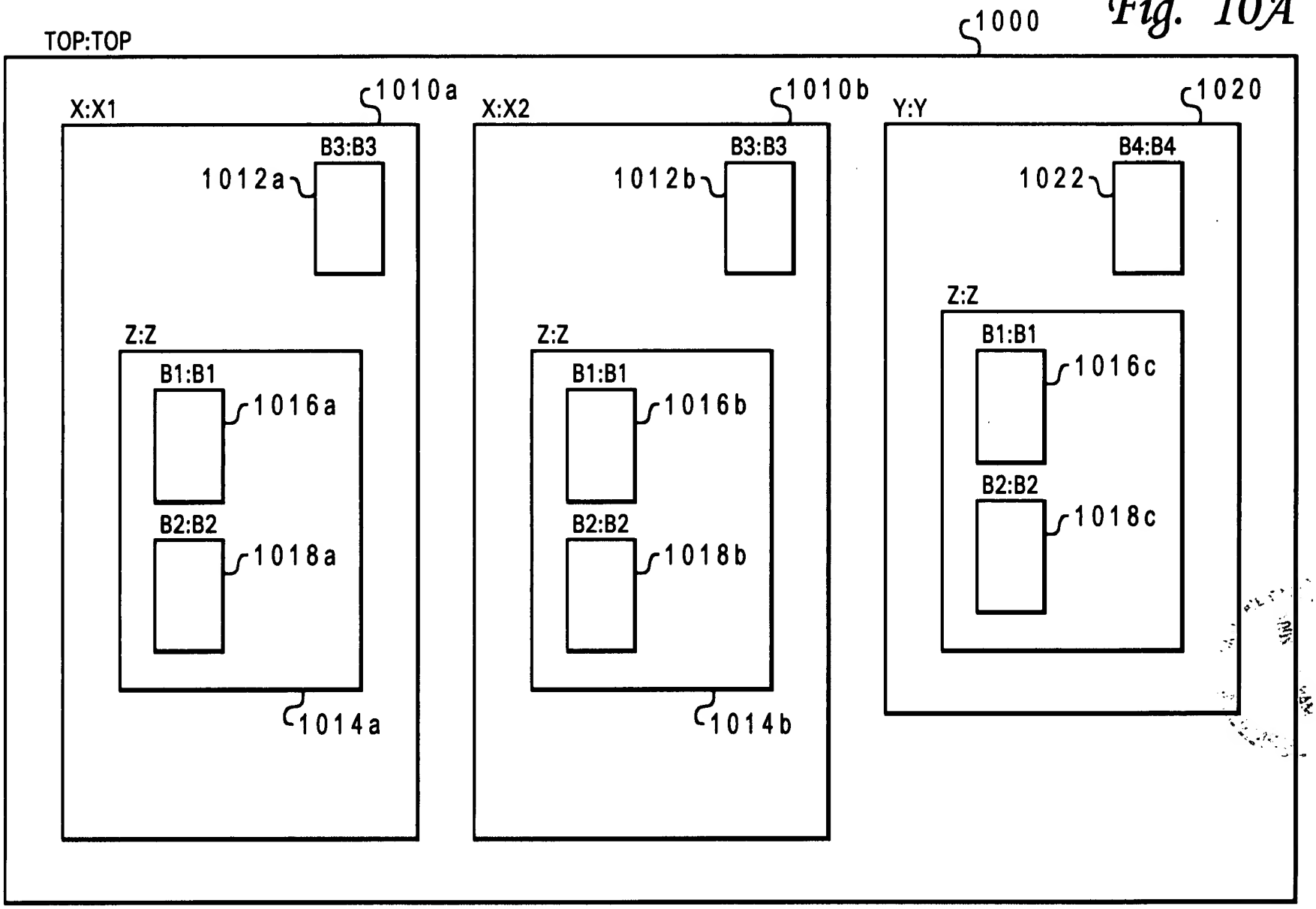
TOP:TOP
1000
X:X1
1010a
B3:B3
1012a
Z:Z
B1:B1
1016a
B2:B2
1018a
1014a
X:X2
1010b
B3:B3
1012b
Z:Z
B1:B1
1016b
B2:B2
1018b
1014b
Y:Y
1020
B4:B4
1022
Z:Z
B1:B1
1016c
B2:B2
1018c

1030 1032 1034 1036

<instantiation identifier>.<instrumentation entity name>.<design entity name>.<eventname>

Fig. 10B

1030	1032	1034	1036	
X1	B3	X	COUNT1	1040
X1.Z	B1	Z	COUNT1	1041
X1.Z	B2	Z	COUNT1	1042
X2	B3	X	COUNT1	1043
X2.Z	B1	Z	COUNT1	1044
X2.Z	B2	Z	COUNT1	1045
Y	B4	Y	COUNT1	1046
Y.Z	B1	Z	COUNT1	1047
Y.Z	B2	Z	COUNT1	1048

Fig. 10C

1030 1034 1036

<instantiation identifier>.<design entity name>.<eventname>

Fig. 10D

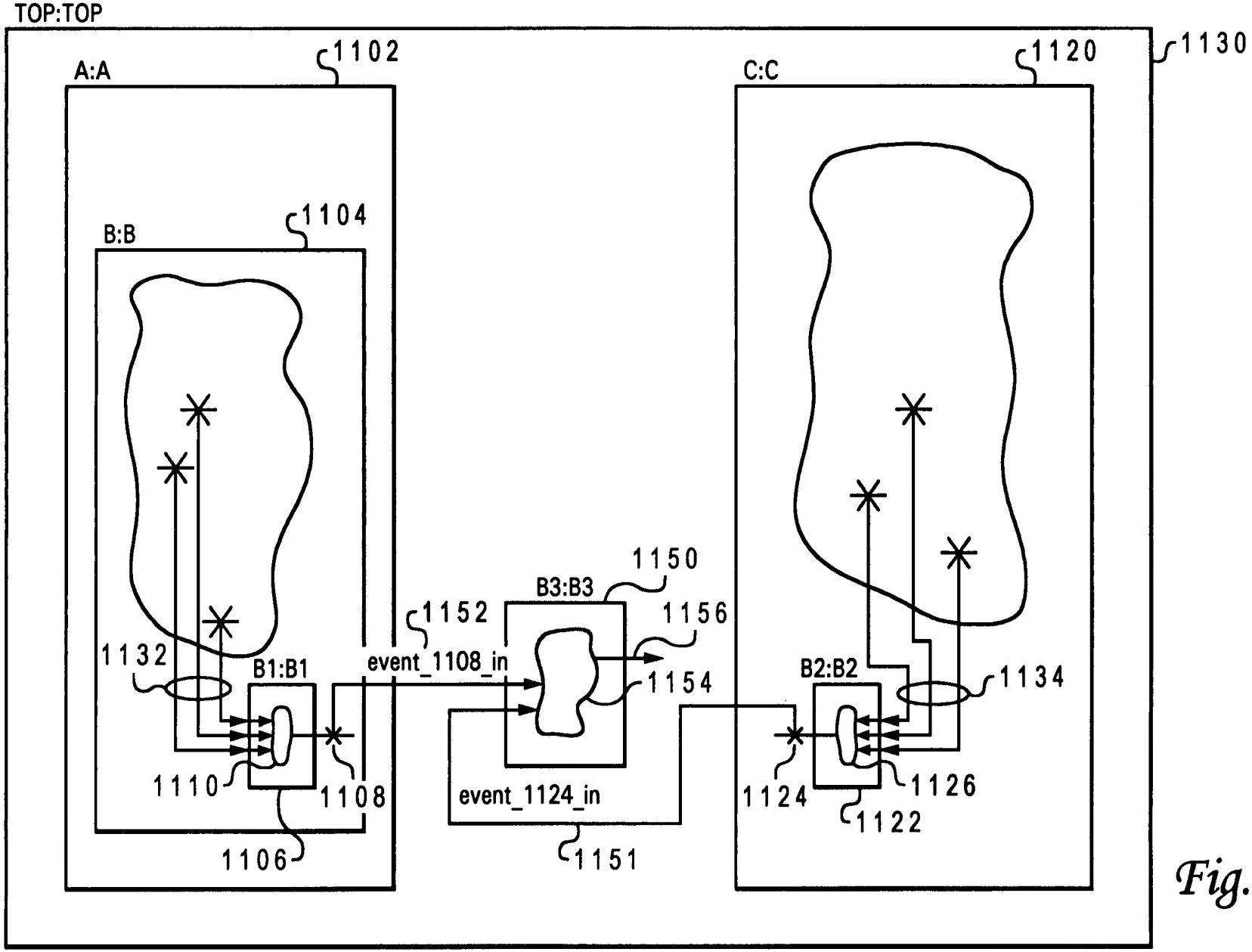
TOP:TOP
A:A
1102
1130
C:C
1120
B:B
1104
1150
B3:B3
1152
1156
1132
B1:B1
event_1108_in
1154
B2:B2
1134
1110
1108
event_1124_in
1124
1126
1122
1106
1151

Fig. 11A

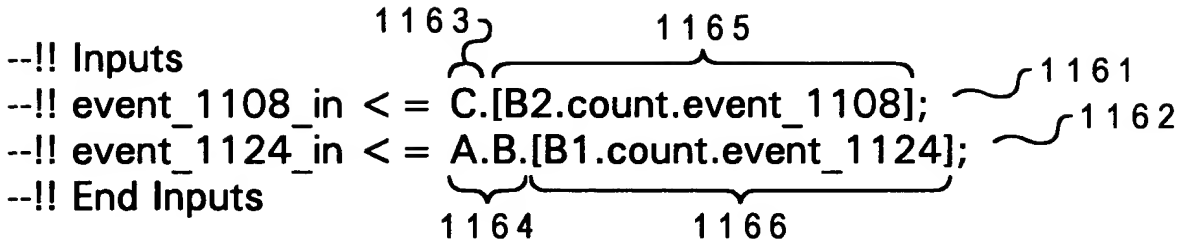

Fig. 11B

```
--!! Inputs
--!! event_1108_in < = C.[count.event_1108];
--!! event_1124_in < = B.[count.event_1124];
--!! End Inputs
```

1171
1172

Fig. 11C